



**Presented to:** Dr. Maher Mansour

**Subject name:** Computer Interface

**Project title:** Garage System

**Team ID:** 3D (C4)


**Team Members:**

- Waleed Ebrahim
- Mohamed Osama Saleh Ahmed
- Youssef Ahmed Hosni
- Helal Omar Helal

## Components:

- 1x Atmega32
- 2x Seven-Segment Display
- 2x LDR
- 2x Laser Module
- 4x LEDs
- 2x 10k $\Omega$  resistors
- 1x Servo Motor
- 2x Breadboards to implement the circuit on
- 1x USB to TTL converter

## Circuit on proteus:

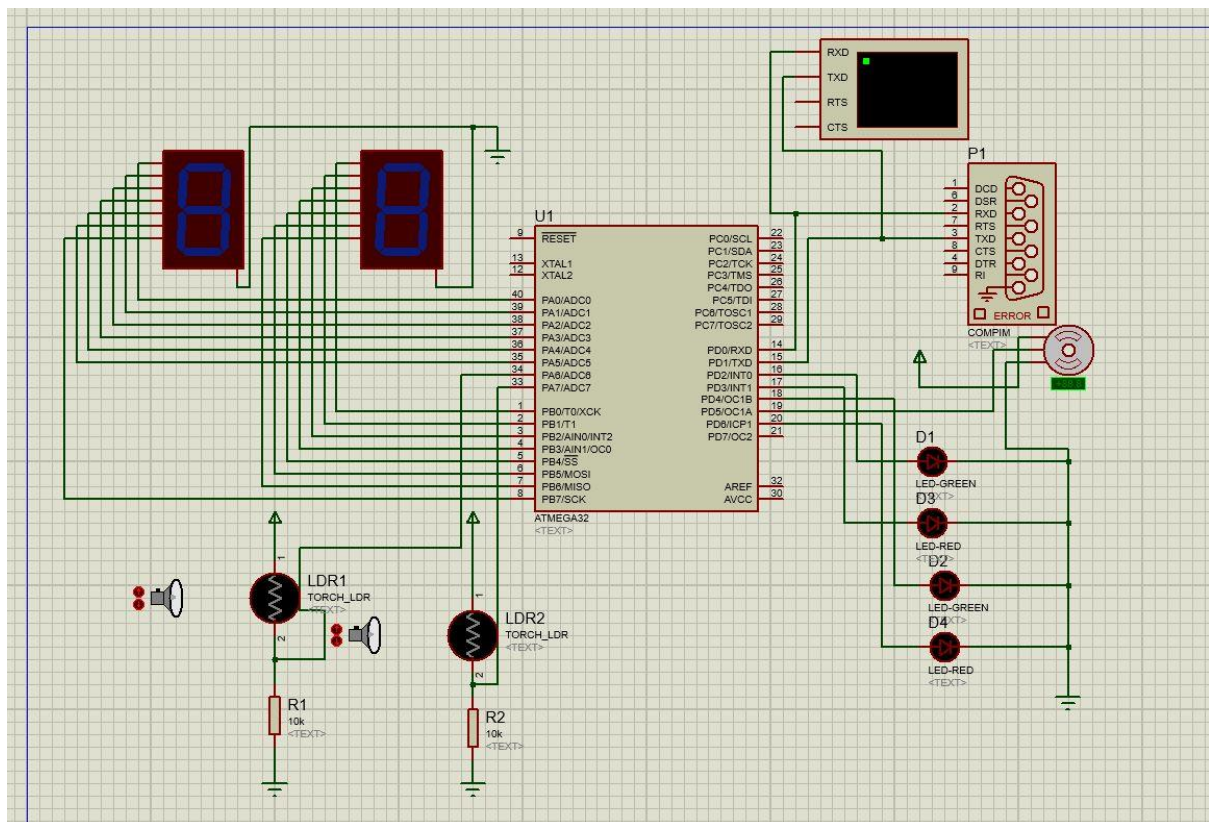

## Role of operation:

### Garage System prototype with two gates

- The **2 LDRs & Laser Modules** detect that a car has passed as when the car passes between both the LDR & Laser; it prevents the LDR from detecting the Laser light.
  - If the car prevents the outer LDR from detecting the laser's light; *Car is entering the garage*
  - If the car prevents the inner LDR from detecting the laser's light; *Car is exiting the garage*
- The **2 Seven-Segments** used to present the number of cars in the garage
- The **4 LEDs** are used to present which direction is used now;
  - the green LED in entrance or exit path indicates that *a car is entering or exiting respectively*
  - the red LED in entrance or exit path indicates that *it's not allowed to enter or exit respectively*
- The **Servo Motor** control the 2 gates which's controlled from the GUI
- The **GUI** is the Servo Motor controller & displays the number of free & busy places
- The **2 Breadboards** is used to implement the circuit on

## Hardware circuit image:

